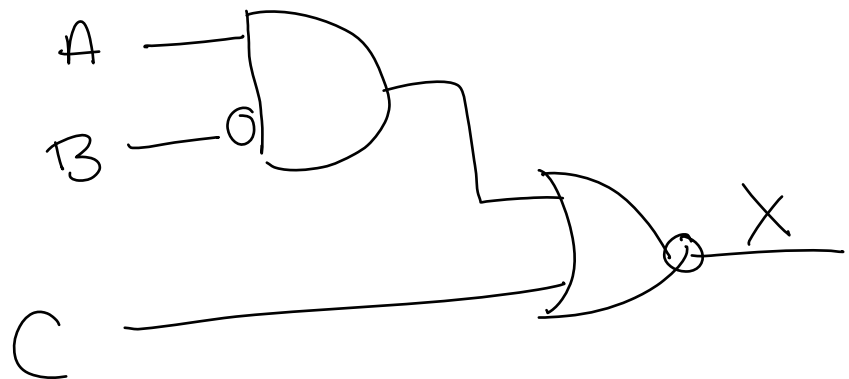


Drawing Logic Gates From Boolean Expression

- Single inverse sign over 1 variable means an inverter on an input.
- Large inverse sign over more than one variable means inverter on the output.

$$(A \bar{B} + C)$$



$$(\overline{ABC} + D) + (\overline{\overline{ABC} + D})$$

