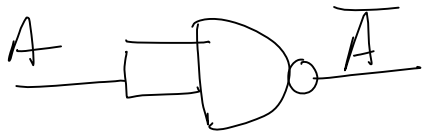



Nand Gate Universal Property

Inverter




A	B	X
0	0	1
0	1	1
1	0	1
1	1	0


AND Gate

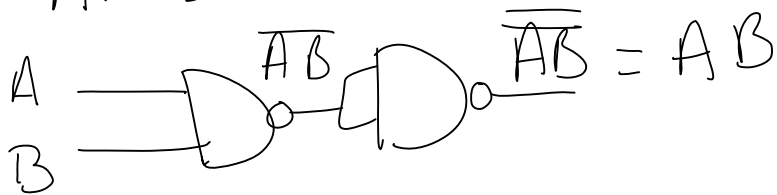

OR Gate

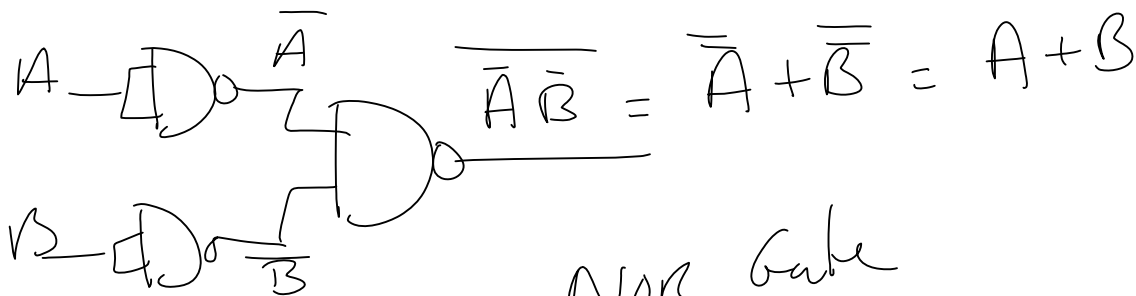

NOR Gate

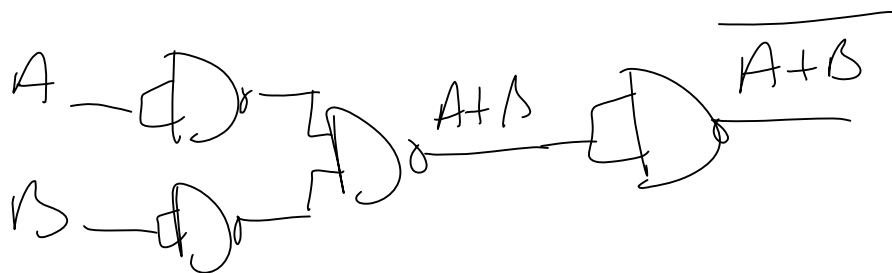

Works Best with SOP Form

$AB + CD$

